

• Objective: To make a digital clock.

• Input Taken: 10MHz Clock, button push. It is vector containing 3 buttons. Use of each button:
~~button(0)~~

When pressed:

button(0): Mode of display can be changed [HH:MM \rightleftharpoons MM:ss]

button(1): Causes change of state from display to allow change of time settings.

button(2): Used for incrementing operation. Considering a normal push ^{comes in} of 0.1sec and more ~~than~~ of that used in fast increment.

Logic of fast increment: For first 0.5sec just normally increment. If button is pressed ~~more~~ than for every 0.2sec increment by 1.

• Output:

i) anode_activate: There are 4 anodes. Each anode decides which number should be refreshed. As at any instant we can just refresh a single digit from the 4. Refresh rate should be between 1ms-16ms so as that human eyes doesn't see a difference between the refreshing. In our circuit, refresh rate is 4ms. i.e. whole cycle takes 4ms (1ms for each digit.)

ii) led: It is the 7 segment display which is seen on the board. Each bit describes a part of the seven lines. Bit set to '0' means to light the led line.

States:

AH \Rightarrow Normal display HH:MM

AS \Rightarrow Normal display MM:SS

~~FH1, FH~~

FH1 \Rightarrow State for increment of unit digits of ^{minute}~~second~~

FH2 \Rightarrow State for increment of 10s digit of minute.

FH3 \Rightarrow state for increment of unit digit of hour

FH4 \Rightarrow State for increment of 10s digit of hour

FS1 \Rightarrow State for increment of unit digit of second


FS2 \Rightarrow State for increment of 10s digit of second

FS3 \Rightarrow state for increment of unit digit of minute

FS4 \Rightarrow state for increment of 10s digit of minute

FH1, FH2, FH3, FH4, FS1, FS2, FS3, FS4 are the intermediate states so that we don't skip the incrementation of any digit. (more clear in state diagram)

Diagram:

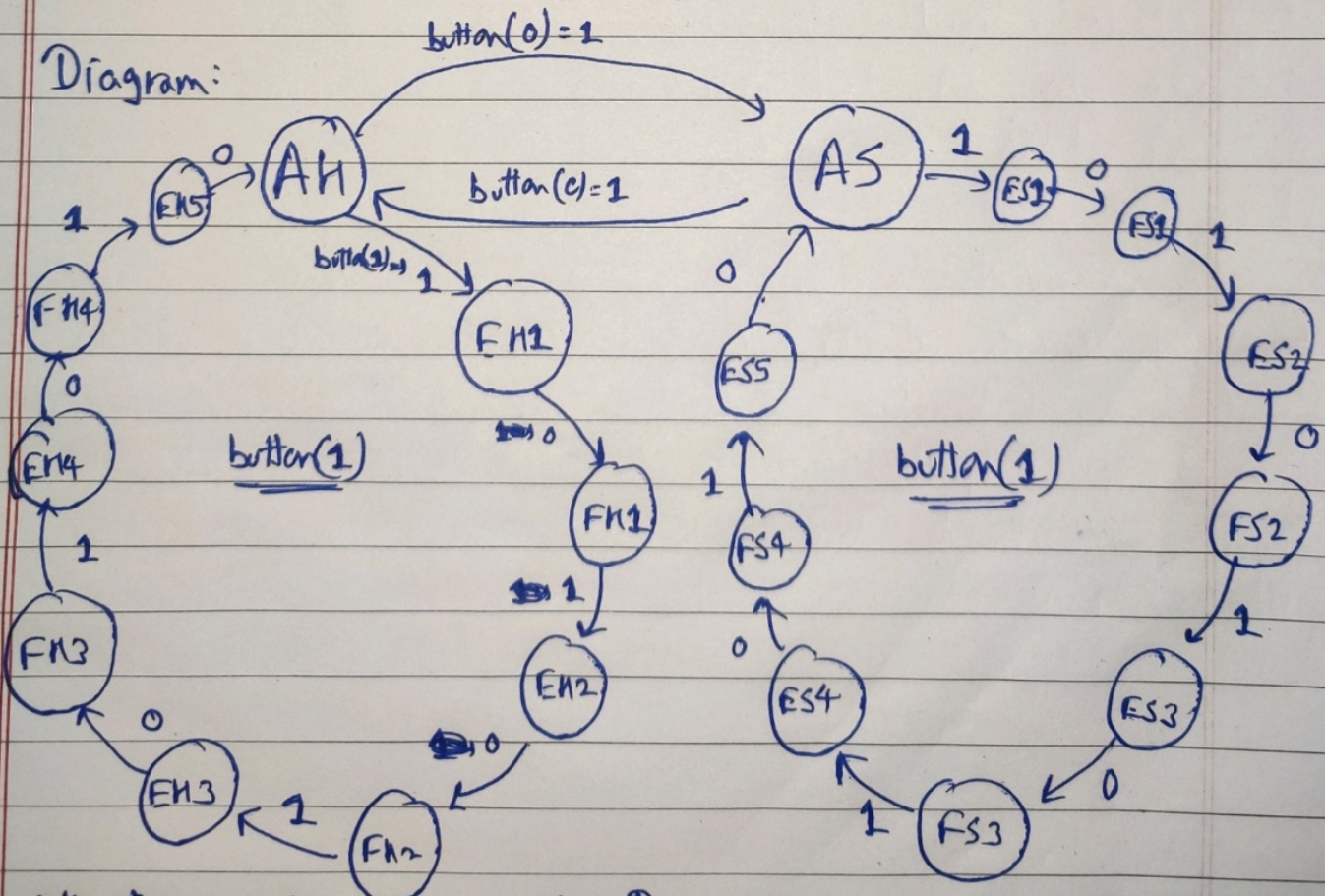

All other transitions other than arrays are to itself.

State Transition:

	Present	button push			Next State
		0	1	2	
Default ①	AH	1	-	-	AS
		0	1	-	EH1
②	AS	1	-	-	AH
		0	1	-	ES1
③	EH1	-	0	-	FH1
④	FH1	-	1	-	EH2
⑤	EH2	-	0	-	FH2
⑥	FH2	-	1	-	EH2
⑦	EH3	-	0	-	FH3
⑧	FH3	-	1	-	EH3
⑨	EH4	-	0	-	FH4
⑩	FH4	-	1	-	EH4
⑪	EH5	-	0	-	AH
⑫	ES1	-	0	-	FS1
⑬	FS1	-	1	-	ES2
⑭	ES2	-	0	-	FS2
⑮	FS2	-	1	-	ES3
⑯	ES3	-	0	-	FS3
⑰	FS3	-	1	-	ES4
⑱	ES4	-	0	-	FS4
⑲	FS4	-	1	-	ES5
⑳	ES5	-	0	-	AS

• Design:

- i) Display entity and its architecture: Its inputs are 10MHz clock and button push. The outputs are given to board to display. anode activate & led. It ~~used~~ uses instance of entity assign, to get the 4 digit number to be displayed. It ~~used~~ uses instance of entity clk_part1ms to get 1ms clock which is used in the process for refresh rate.
- ii) Assign entity and its architecture: It gets clk and buttons as input and gives displayed number as output. It uses all the states describe before to generate the desired output. It ~~used~~ uses clk_part1 entity to get 1sec clock for normal ticking of the clock. Bit vectors $s_0, s_1, m_0, n_1, n_0, n_2$ are used for working which form the displayed number depending on state.
- iii) clk_part1 entity and ~~design~~ ^{arch}: It gets the 10MHz clock as input and gives 1^{Hz} clock as output. We start a counter and when counter reaches 4999999, the 1Hz clock changes its value. (low becomes high, high becomes low). As 0 to 4999999 means 5×10^6 rising edges so half period.
- iv) clk_part0.1s entity & design: It gets 10MHz clock as input and gives 10Hz i.e. 0.1sec clock as output. Same working as clk_part1, just counter reaches 499999.
- v) clk_part1ms entity & arch: It gets 10MHz clock as input and gives 10^3 Hz i.e. 1ms clock as output. Same working. Just counter reaches 4999.